

Problem 7.27 Determine the equivalent impedance:

- (a) Z_1 at 1000 Hz (Fig. P7-27)(a))
- (b) Z_2 at 500 Hz (Fig. P7-27)(b))
- (c) Z_3 at $\omega = 10^6$ rad/s (Fig. P7-27)(c))
- (d) Z_4 at $\omega = 10^5$ rad/s (Fig. P7-27)(d))
- (e) Z_5 at $\omega = 2000$ rad/s (Fig. P7-27)(e))


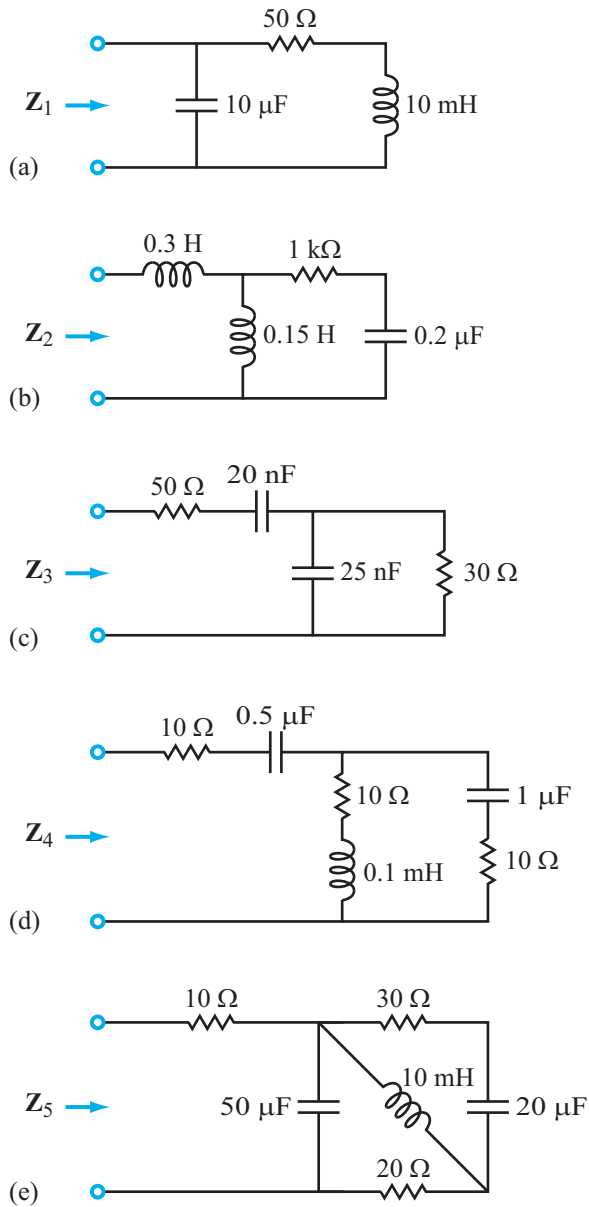


Figure P7.27: Circuit for Problem 7.27.

Solution:

(a)

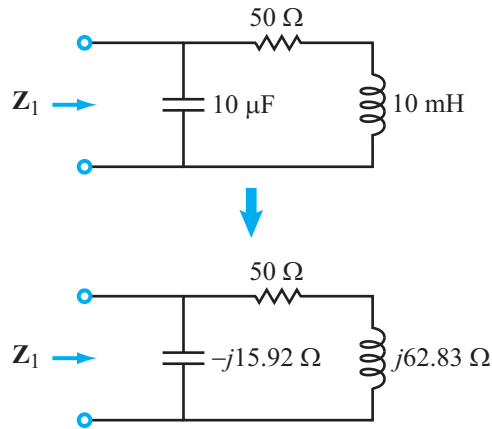


$$\mathbf{Z}_C = \frac{-j}{\omega C} = \frac{-j}{2\pi \times 10^3 \times 10 \times 10^{-6}} = -j15.92 \Omega$$

$$\mathbf{Z}_L = j\omega L = j2\pi \times 10^3 \times 10^{-2} = j62.83 \Omega$$

$$\begin{aligned} \mathbf{Z}_1 &= (50 + j62.83) \parallel (-j15.92) \\ &= \frac{(50 + j62.83)(-j15.92)}{50 + j62.83 - j15.92} \\ &= \frac{1000 - j796}{50 + j46.91} \cdot \left(\frac{50 - j46.91}{50 - j46.91} \right) \\ &= \frac{12660 - j86710}{4701} = (2.7 - j18.5) \Omega. \end{aligned}$$

(b)

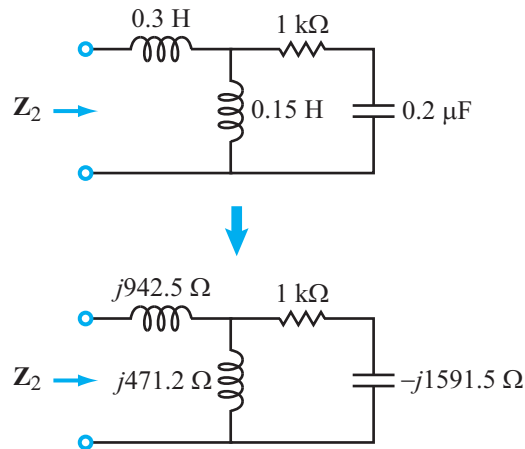



$$\mathbf{Z}_{L_1} = j\omega L_1 = j2\pi \times 500 \times 0.3 = j942.5 \Omega$$

$$\mathbf{Z}_{L_2} = j\omega L_2 = j471.2 \Omega$$

$$\mathbf{Z}_C = \frac{-j}{\omega C} = \frac{-j}{2\pi \times 500 \times 0.2 \times 10^{-6}} = -j1591.5 \Omega$$

$$\begin{aligned} \mathbf{Z}_2 &= j942.5 + j471.2 \parallel (1000 - j1591.5) \\ &= j942.5 + \frac{j471.2(1000 - j1591.5)}{1000 - j1591.5 + j471.2} = (98.5 + j1524.0) \Omega \end{aligned}$$

(c)

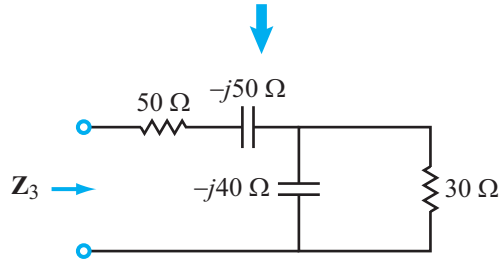
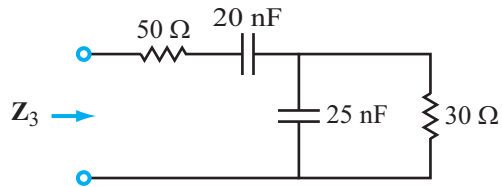


$$\mathbf{Z}_{C_1} = \frac{-j}{\omega C_1} = \frac{-j}{10^6 \times 20 \times 10^{-9}} = -j50 \Omega$$

$$\mathbf{Z}_{C_2} = \frac{-j}{\omega C_2} = \frac{-j}{10^6 \times 25 \times 10^{-9}} = -j40 \Omega$$

$$\mathbf{Z}_3 = 50 - j50 + \frac{30 \times (-j40)}{30 - j40} = (69.2 - j64.4) \Omega.$$

(d)

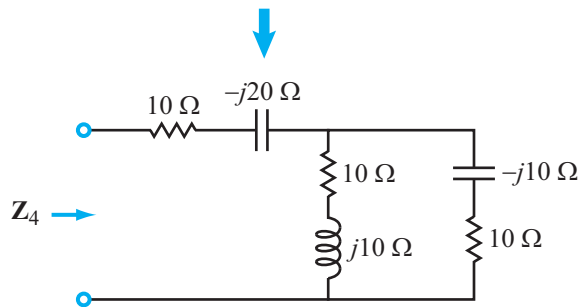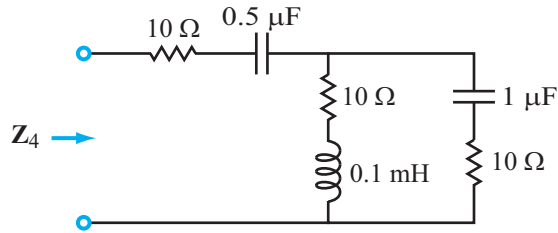






$$\mathbf{Z}_{C_1} = \frac{-j}{\omega C_1} = \frac{-j}{10^5 \times 0.5 \times 10^{-6}} = -j20 \Omega$$

$$\mathbf{Z}_{C_2} = \frac{-j}{\omega C_2} = -j10 \Omega$$

$$\mathbf{Z}_L = j\omega L = j \times 10^5 \times 10^{-4} = j10 \Omega$$

$$\mathbf{Z}_4 = (10 - j20) + \frac{(10 + j10)(10 - j10)}{10 + j10 + 10 - j10} = (10 - j20) + 10 = (20 - j20) \Omega.$$

(e)

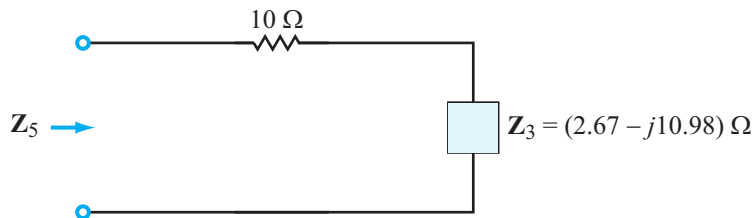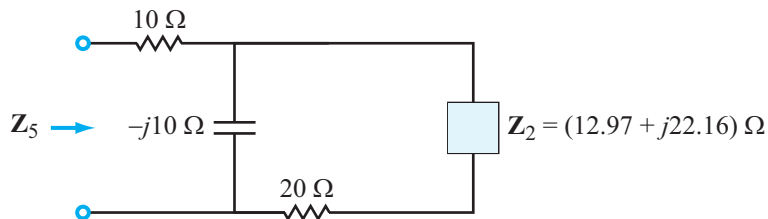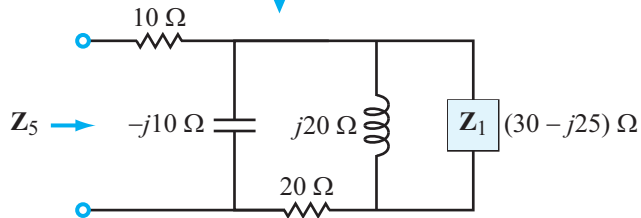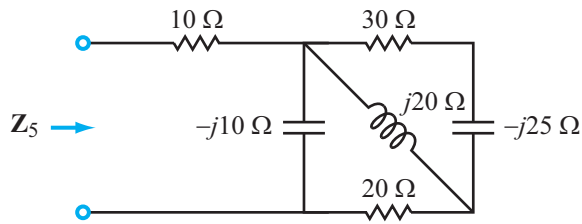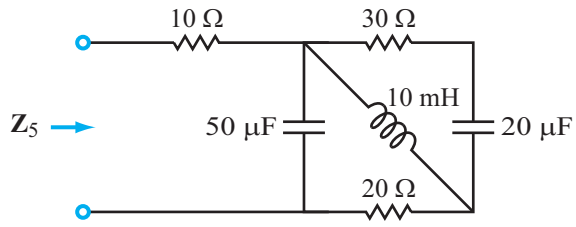

$$\mathbf{Z}_{C_1} = \frac{-j}{\omega C_1} = \frac{-j}{2000 \times 50 \times 10^{-6}} = -j10 \Omega$$

$$\mathbf{Z}_{C_2} = \frac{-j}{\omega C_2} = \frac{-j}{2000 \times 20 \times 10^{-6}} = -j25 \Omega$$

$$\mathbf{Z}_L = j\omega L = j2000 \times 10 \times 10^{-3} = j20 \Omega$$

$$\mathbf{Z}_2 = \mathbf{Z}_1 \parallel (j20)$$

$$= \frac{(30 - j25)(j20)}{30 - j25 + j20}$$

$$= \frac{500 + j600}{30 - j5} \cdot \frac{(30 + j5)}{(30 + j5)}$$

$$= \frac{12000 + j20500}{925} = (12.97 + j22.16) \Omega$$

$$\mathbf{Z}_3 = (20 + \mathbf{Z}_2) \parallel (-j10)$$

$$= \frac{(32.97 + j22.16)(-j10)}{32.97 + j22.16 - j10}$$

$$= \frac{221.6 - j329.7}{32.97 + j12.16} \cdot \frac{(32.97 - j12.16)}{(32.97 - j12.16)}$$

$$= (2.67 - j10.98) \Omega$$

$$\mathbf{Z}_5 = 10 + \mathbf{Z}_3 = (12.67 - j10.98) \Omega.$$

Problem 7.31 In response to an input signal voltage $v_s(t) = 24 \cos 2000\pi t$, the input current in the circuit of Fig. P7.31 was measured as $i(t) = 6 \cos(2000\pi t - 60^\circ)$ mA. Determine the equivalent input impedance \mathbf{Z} of the circuit.

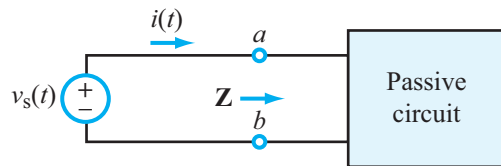


Figure P7.31: Configuration for Problem 7.31.

Solution:

$$\mathbf{V}_s = 24 \text{ V},$$

$$\mathbf{I} = 6e^{-j60^\circ} \quad (\text{mA}).$$

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}}$$


$$= \frac{24}{6e^{-j60^\circ} \times 10^{-3}}$$

$$= 4e^{j60^\circ} \text{ k}\Omega$$

$$= (4 \cos 60^\circ + j4 \sin 60^\circ) \text{ k}\Omega = (2 + j3.46) \text{ k}\Omega.$$

Problem 7.52 Apply mesh analysis to determine \mathbf{I}_C in the circuit of Fig. P7.51.

Solution:

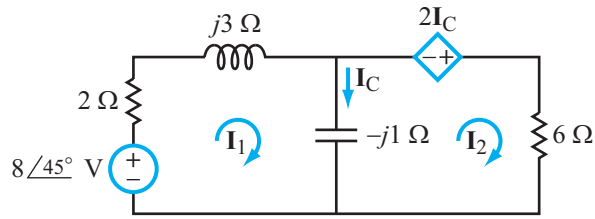

$$\begin{aligned} -8e^{j45^\circ} + 2\mathbf{I}_1 + j3\mathbf{I}_1 - j1(\mathbf{I}_1 - \mathbf{I}_2) &= 0 \\ -j1(\mathbf{I}_2 - \mathbf{I}_1) - 2\mathbf{I}_C + 6\mathbf{I}_2 &= 0 \end{aligned}$$

Also,

$$\mathbf{I}_C = \mathbf{I}_1 - \mathbf{I}_2.$$

Solution gives

$$\mathbf{I}_1 = \frac{64 - j8}{19 + j16} e^{j45^\circ} \quad (\text{A}) \qquad \mathbf{I}_2 = \frac{16 - j8}{19 + j16} e^{j45^\circ} \quad (\text{A})$$

$$\mathbf{I}_C = \mathbf{I}_1 - \mathbf{I}_2 = \frac{48e^{j45^\circ}}{19 + j16} = 1.93e^{j4.9^\circ}.$$

Problem 7.53 Apply mesh analysis to determine $i_L(t)$ in the circuit of Fig. P7.53.


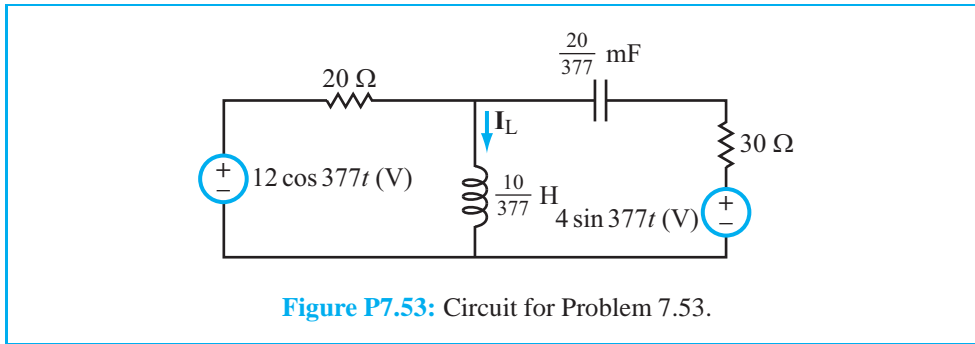


Figure P7.53: Circuit for Problem 7.53.

Solution:

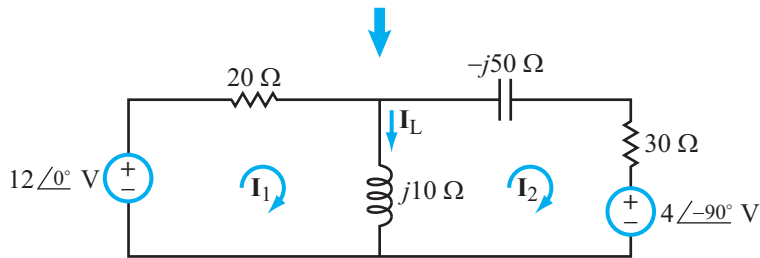

$$12 \cos 377t \Rightarrow 12 \angle 0^\circ$$

$$4 \sin 377t \Rightarrow 4 \angle -90^\circ$$

$$\mathbf{Z}_C = \frac{-j}{\omega C} = \frac{-j}{377 \times \frac{50}{377}} = -j50 \Omega$$

$$\mathbf{Z}_L = j\omega L = j377 \times \frac{10}{377} = j10 \Omega$$

Mesh 1:

$$-12 + 20\mathbf{I}_1 + j10(\mathbf{I}_1 - \mathbf{I}_2) = 0$$

Mesh 2:

$$j10(\mathbf{I}_2 - \mathbf{I}_1) - j50\mathbf{I}_2 + 30\mathbf{I}_2 + 4e^{-j90^\circ} = 0$$

Solution leads to

$$\mathbf{I}_1 = 0.48e^{-j31.87^\circ} \quad (\text{A}), \quad \mathbf{I}_2 = 0.17e^{j125.75^\circ} \quad (\text{A}),$$


$$\mathbf{I}_L = \mathbf{I}_1 - \mathbf{I}_2$$

$$= 0.64e^{-j37.66^\circ}$$

$$i_L(t) = \Re\{\mathbf{I}_L e^{j377t}\}$$

$$= 0.64 \cos(377t - 37.66^\circ) \quad (\text{A}).$$

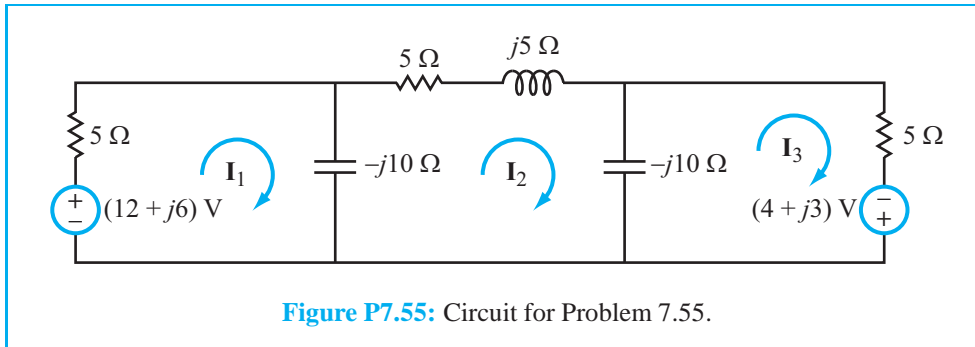Problem 7.55 Apply the by-inspection method to develop a mesh-current matrix equation for the circuit in Fig. P7.55, and then use MATLAB® software to solve for \mathbf{I}_1 , \mathbf{I}_2 , and \mathbf{I}_3 .



Solution:

$$\begin{bmatrix} (5 - j10) & j10 & 0 \\ j10 & (5 + j5 - j10) & j10 \\ 0 & j10 & (5 - j10) \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 12 + j6 \\ 0 \\ 4 + j3 \end{bmatrix}$$


MATLAB® software solution gives

$$\mathbf{I}_1 = (0.38 + j0.42) \text{ A}$$


$$\mathbf{I}_2 = (0.77 - j0.59) \text{ A}$$

$$\mathbf{I}_3 = (0.30 - j0.34) \text{ A}$$

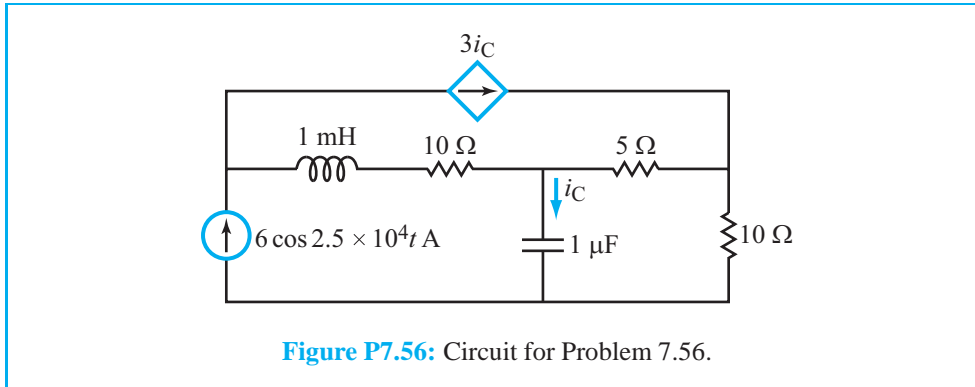Problem 7.56 Use any analysis technique of your choice to determine $i_C(t)$ in the circuit of Fig. P7-56.



Solution:

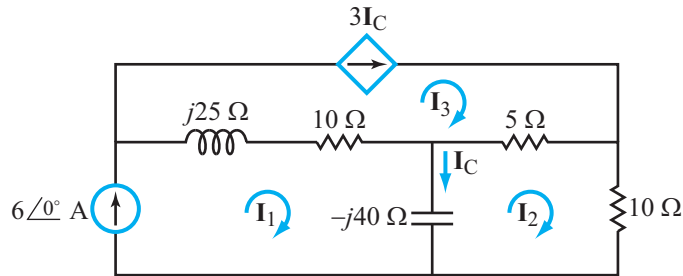

$$Z_L = j\omega L = j2.5 \times 10^4 \times 10^{-3} = j25 \Omega$$

$$Z_C = \frac{-j}{\omega C} = \frac{-j}{2.5 \times 10^4 \times 10^{-6}} = -j40 \Omega$$

The mesh-current method gives:

$$\begin{aligned} \text{Mesh 1:} & \quad \mathbf{I}_1 = 6 \text{ A} \\ \text{Mesh 2:} & \quad -j40(\mathbf{I}_2 - \mathbf{I}_1) + 5(\mathbf{I}_2 - \mathbf{I}_3) + 10\mathbf{I}_2 = 0 \\ \text{Mesh 3:} & \quad \mathbf{I}_3 = 3\mathbf{I}_C \\ \text{Auxiliary:} & \quad \mathbf{I}_C = \mathbf{I}_1 - \mathbf{I}_2. \end{aligned}$$

Simultaneous solution leads to

$$\mathbf{I}_1 = 6 \text{ A}, \quad \mathbf{I}_2 = (4.92 - j1.44) \text{ A}.$$

$$\begin{aligned} \mathbf{I}_C &= \mathbf{I}_1 - \mathbf{I}_2 \\ &= 1.8e^{j53.13^\circ} \text{ A}. \end{aligned}$$

$$\begin{aligned} i_C(t) &= \Re\{\mathbf{I}_C e^{j\omega t}\} \\ &= 1.8 \cos(2.5 \times 10^4 t + 53.13^\circ) \quad (\text{A}). \end{aligned}$$

Problem 7.57 Determine $i_x(t)$ in the circuit of Fig. P7.57, given that $v_s(t) = 6\cos 5 \times 10^5 t$ V.


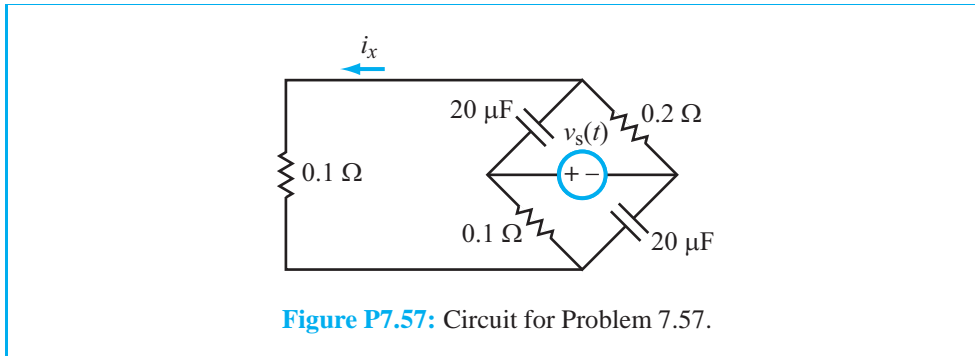


Figure P7.57: Circuit for Problem 7.57.

Solution:

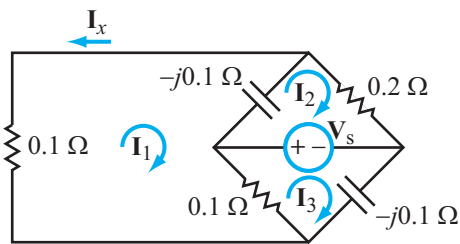

At $\omega = 5 \times 10^5$ rad/s,

$$\mathbf{Z}_C = \frac{-j}{\omega C} = \frac{-j}{5 \times 10^5 \times 20 \times 10^{-6}} = -j0.1 \Omega$$

$$\mathbf{V}_s = 6\angle 0^\circ \text{ V}$$

Application of the mesh current by inspection method gives:

$$\begin{bmatrix} (0.1 + 0.1 - j0.1) & j0.1 & -0.1 \\ j0.1 & (0.2 - j0.1) & 0 \\ -0.1 & 0 & (0.1 - j0.1) \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 6 \\ -6 \end{bmatrix}$$

Solution of matrix equation gives

$$\mathbf{I}_1 = (6.79 - j23.77) \text{ A}$$

$$\mathbf{I}_2 = (15.85 - j4.53) \text{ A}$$

$$\mathbf{I}_3 = -(14.72 + j38.49) \text{ A}$$

$$\mathbf{I}_x = -\mathbf{I}_1 = (6.79 - j23.77) \text{ A} = 24.72e^{-j74.06^\circ} \text{ A}$$

$$i_x(t) = 24.72 \cos(5 \times 10^5 t - 74.06^\circ) \text{ A.}$$